



# Department of Electronic and Telecommunication Engineering

## University of Moratuwa

**EN2111 Electronic Circuit Design**

**Linear Power Supply - Group 37**

<b>Pushpakumara.H.M.R.M.</b>	<b>200488E</b>
<b>Morawaka M.D.</b>	<b>200400F</b>
<b>Himeka S.H.D.</b>	<b>200222K</b>


$$37 \bmod 5 \Rightarrow 2$$

$$\text{mid Input } V = 16$$

$$\begin{aligned}\text{mid output } V &= 16 - 8 + (37 \bmod 3) \\ &= 8 + 1 \\ &= 9 \quad \pm 3\end{aligned}$$

Input Voltage Range :  $16 \pm 2$   
 $14 - 18 \text{ V}$

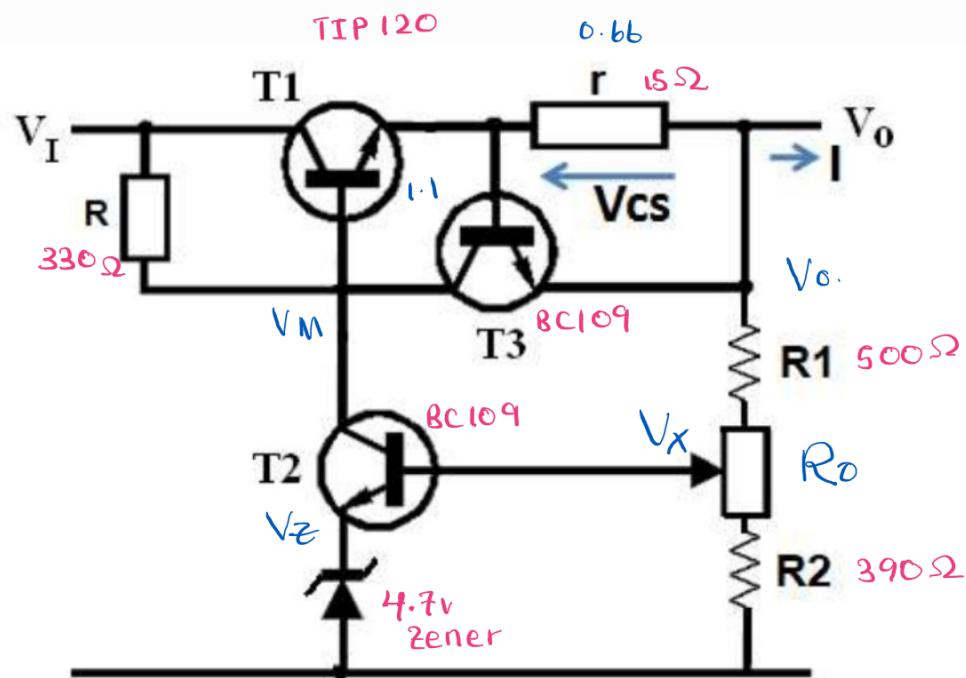Output Voltage Range :  $9 \pm 3$   
 $6 - 12 \text{ V}$



Given data:

$$T_2 \rightarrow BC109$$

$$T_3 \rightarrow BC109$$

$$\text{max. } I = 100 \text{ mA}$$

## ① Calculations & component selection.

### • $T_1$ (pass element)

We need to find maximum power dissipation through  $T_1$  (pass element)

$$P = (V_{CE\ max}) (I_{max})$$

$$= (18 - 6) \text{ V} \times 0.1 \text{ A}$$

$$= 1.2 \text{ W}$$

So we had to select a transistor with maximum power rating more than 1.2W

We found TIP 120 for  $T_1$  which had a power dissipation of 2W

$$T_1 \rightarrow TIP 120$$

Derate above 25°C		0.52	W/°C
Total Power Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	$P_D$	2.0 0.016	Watts W/°C
Unclamped Inductive Load Energy (1)	E	50	mJ

- zenor diode

since our minimum output voltage was 6V

We needed  $V_Z$  to be less than 5.3V  
 $\therefore (6V - 0.7V)$ .

$\therefore$  Our selected zener  $\text{IN4732}$   
 which had 4.7 zener voltage

- $R_1$  and  $R_2$

We kept the value of  $R_1$  fixed

$$R_1 \rightarrow 500\Omega$$

and selected zener  $V_Z \Rightarrow 4.7V$

$T_2$  is a BC109; and it's always on active region

$$V_x = 4.7 + 0.7 = 5.4$$

$$5.4 = \left( \frac{R_T}{0.5 + R_T} \right) 6$$

$$5.4 = \left( \frac{R_T}{0.5 + R_T} \right) 12$$

$$\frac{5.4}{2} + 5.4 R_F = 6 R_F$$

$$\frac{5.4}{2} + 5.4 R_{T_{min}} = 12 R_T$$

$$R_F \max = 4.5k\Omega$$

$$R_T \min = 400\Omega$$

since

$$R \rightarrow 500\Omega$$

We needed  $R_O + R_2 = R_T$  to vary between  $400\Omega$  to  $4.5k\Omega$ . Approximately we used  $390\Omega$  for  $R_2$  and a  $10K$  potentiometer.

$R_T$  vary  $\Rightarrow 390 + 10K$

- $r$  in the current limiting circuit

Since we used BC109 for  $T_2$

$r$  was calculated as follows

$$V_{BE \text{ cutoff}} = I_{max} R$$

$$0.66 = 0.1 \times r \\ r = 6.6\Omega$$

- $R$   $V_{BE}$  of TIP120  $\rightarrow 1.1V$

$$\frac{V_{Imin} - V_{m max}}{R} > I_{test \text{ zenor}}$$

$$\frac{14 - (12 + 0.66 + 1.1)}{R} > 1 \text{ mA}$$

$$R < 300\Omega$$

We approximately used  $330\Omega$  for  $R_1$

## ② Observations

since the output current was limited to 98 mA we had to use  $15\Omega$  resistor for the resistor

- \* Line variation was around 0.01 V per 1 V input voltage variation
- \* Output current was limited at 0.098 A<sub>II</sub>


(2)

## Voltage , Current Vs Load Graphs.

Load variation

We fixed the input Voltage to 18v


Load ( $\Omega$ )	Output (V)
3.3	6.3346
3.9	6.3830
5.6	6.5488
6.2	6.37
14.7	2.11
36	3.89
51.6	5.28
65.58	7.48
100	8.61
115	9.32
114	9.75
167	9.80
191	9.94
232	10
334	10

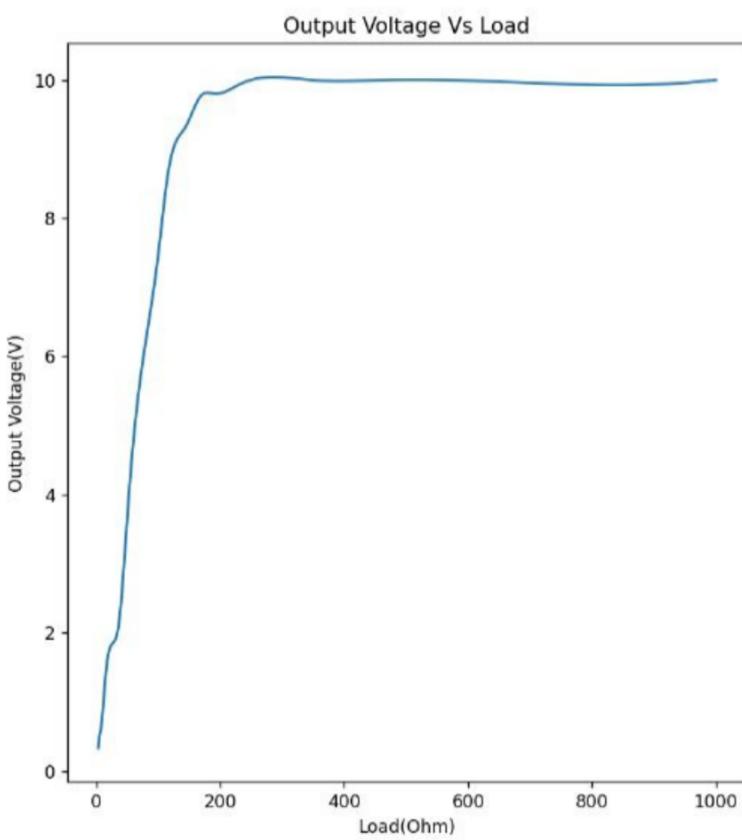

## Line Variation

$$-0.01 \text{ V}/\text{V}$$

Input V (V)	Output (V)
14	10.012
14.5	10.018
15	10.021
15.5	10.024
16.	10.033
16.5	10.037
17	10.041
17.5	10.044
18	10.052

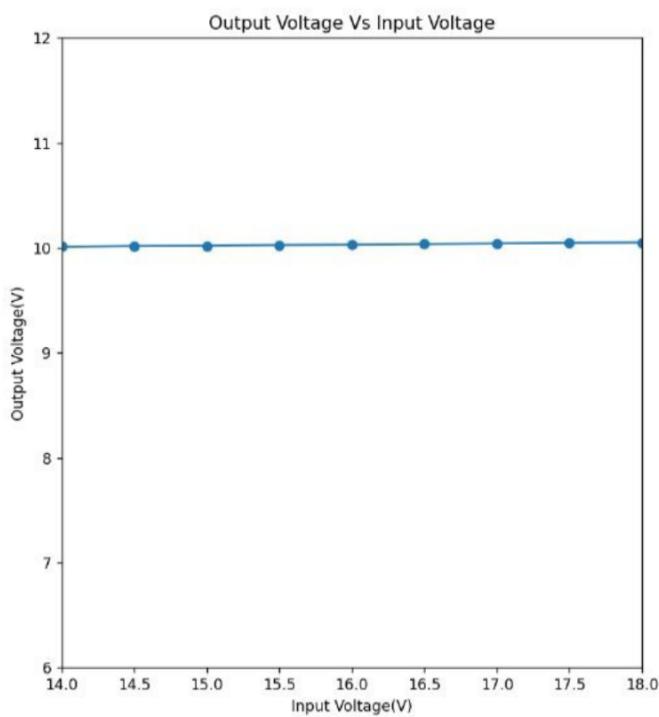

## Our circuit

